

Jiovany Soliman, 1951338

Chloe' Miller, 2031648

EE/CSE 371 Lab 4 Report: Implementing Algorithms in Hardware

November 06, 2023

## Design Procedure

The purpose of this lab was to implement algorithms in hardware by translating ASMD charts to code in SystemVerilog. We first implemented a circuit that counts the number of bits set to 1 in an n-bit input A by combining the necessary datapath components and a control circuit FSM. This circuit also displayed the number of 1's counted in A on the 7-segment HEX displays and lit an LED to indicate whenever the algorithm had finished. We then implemented a binary search algorithm, which searches through an unsigned sorted array to locate an 8-bit value A once the user presses Start. Rather than compare each value in the array to the target value, the algorithm simply compares the target value to the middle value between two bounds of the array and determines if it needs to keep searching in the first or second half of the array, repeatedly comparing the target value to the middle value between the two bounds. Lastly, we combined the functionalities of these two algorithms by adding a switch that the user could toggle to run either the bit-counting or the binary search algorithm.

### Task #1:

For task 1, we referenced the provided ASM chart to identify our control, status, and external input signals. Then, we added to the ASM chart these signals and RTL to develop the ASMD chart needed for implementing the control and datapath in SystemVerilog. This task was straightforward and did not take much time to code.

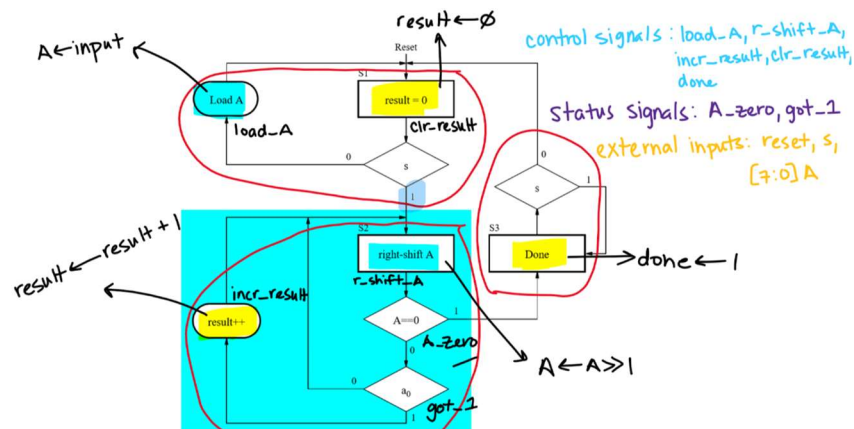


Figure 1: Algorithmic State Machine with Datapath (ASMD) chart for a bit-counting circuit. Note that this diagram as-is is not sufficient for your lab report; please follow the ASMD chart style shown in lecture.

Figure 1: ASMD chart for task 1

```

1  /*
2  Module to implement the control path of task 1.
3  External inputs (inputs): clk, reset, s
4  Status signals (inputs): A_zero (true if A = 0, false otherwise), got_1 (true if A[0] = 1, false otherwise)
5  Control signals (outputs): load_A, r_shift_A, incr_result, clr_result, done
6  */
7
8  module counter_cntrl(clk, reset, s, A_zero, got_1, load_A, r_shift_A, incr_result, clr_result, done);
9
10 // port definitions
11 input logic clk, reset, s, A_zero, got_1;
12 output logic load_A, r_shift_A, incr_result, clr_result, done;
13
14 // define state names and variables
15 enum {s1, s2, s3} ps, ns;
16
17 // controller logic with synchronous reset
18 always_ff @(posedge clk)
19     if(reset)
20         ps <= s1;
21     else
22         ps <= ns;
23
24 // next state logic
25 always_comb
26     case(ps)
27         s1: ns = s ? s2 : s1;
28         s2: ns = A_zero ? s3 : s2;
29         s3: ns = s ? s3 : s1;
30     endcase
31
32 // output assignments
33 assign load_A      = (ps == s1) & ~s;
34 assign r_shift_A   = (ps == s2);
35 assign incr_result = (ps == s2) & got_1;
36 assign clr_result  = (ps == s1);
37 assign done        = (ps == s3);
38
39 endmodule // counter_cntrl
40

```

Figure 2: Snippet of module counter\_cntrl showing the control path of task 1

```

1  /*
2  External inputs (inputs): clk, A
3  Control signals (inputs): load_A, r_shift_A, incr_result, clr_result
4  Status signals (outputs): A_zero (true if A = 0, false otherwise), got_1 (true if A[0] = 1, false otherwise)
5  External outputs (outputs): result
6  */
7
8  module counter_datapath(clk, A, load_A, r_shift_A, incr_result, clr_result, A_zero, got_1, result);
9
10 // port definitions
11 input logic clk, load_A, r_shift_A, incr_result, clr_result;
12 input logic [7:0] A;
13 output logic [3:0] result; // highest value counter can be is 8
14 output logic A_zero, got_1;
15
16 logic [7:0] a;
17
18 // datapath logic
19 always_ff @(posedge clk) begin
20     if(load_A)
21         a <= A;
22
23     if(clr_result)
24         result <= 0;
25     else if(incr_result)
26         result <= result + 1;
27     else
28         result <= result;
29
30     if(r_shift_A)
31         a <= (a >> 1);
32 end
33
34 assign A_zero = (a == 8'b0);
35 assign got_1 = (a[0] == 1'b1);
36
37 endmodule // counter_datapath
38

```

Figure 3: Snippet of module counter\_datapath showing the data path of task 1



Figure 4: Snippet of task 1 model sim showing result "r" equals 2 reflecting the correct number of bits set to 1 in A.

In ModelSim, we tested our bit-counter algorithm by assigning different values to 8-bit input A, and monitored the result "r", which indicated how many bits were set to 1 in our input. We can see in the waveform above that "r" provides the correct number of 1 bits for both of our inputs of  $A = 3$  and  $A = 5$  in binary, respectively.

## Task #2:

For task 2, we needed to instantiate a 32x8 1-port RAM using a .mif file that we initialized with 32 sorted unsigned values. We then had to implement a binary search algorithm in hardware. We started by drafting an ASMD chart. The first step was to understand our control path that would later be implemented in code using a finite state machine. After we established our control path portion of the ASMD diagram, we started writing down our RTL, which would then be used to establish and implement our data path. It was very helpful to start by drawing the ASMD chart as it clarified our states, control signals, status signals, and finally our RTL. For the algorithm portion, we utilized the commonly used binary search algorithm that's available at a variety of sources online. The main idea is that you start by checking the middle value of your search space to see if it matches your target value. Afterwards, since the search space is assumed to be sorted, you can simply determine if the target value is before the middle value or after the middle value. Once you identify which half of the search space your value is predicted to be in, you update the edges/limits of your search space to only reflect that new half. Afterwards you again select the middle value of that search space and compare it to your target value. You repeat these steps recursively until you either find your target value at which point you break out of the loop, or until you exhaust the entirety of your search space; which can be checked by comparing the 2 limits of your search space to each other. Finally, we had to include 3 additional states for timing purposes.

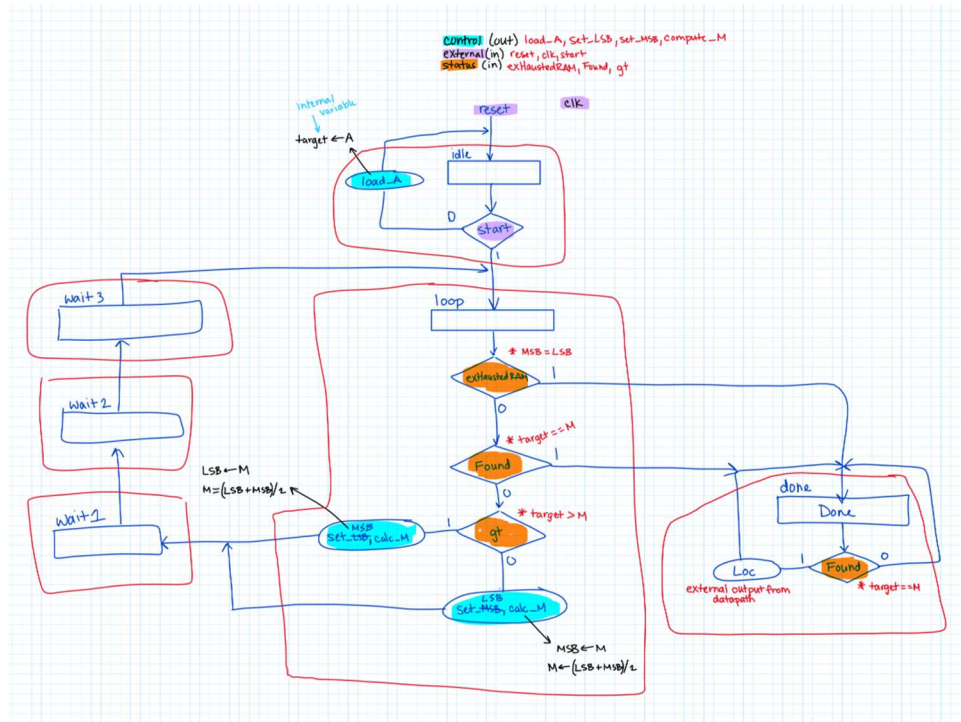


Figure 5: ASMD chart for task 2

```

1 // Module to implement the finite state machine (control path) portion of task 2, the binary search algorithm.
2 // CLOCK_50, Reset, Start, exhaustedRAM, Found, gt are single bit inputs.
3 // Compute_M, Set_LSB, Set_MSB, init are single bit outputs.
4 timescale 1 ps / 1 ps
5 module binaryFSM (CLOCK_50, Reset, Start, exhaustedRAM, Found, gt, Compute_M, Set_LSB, Set_MSB, init);
6 // external inputs
7 input logic CLOCK_50;
8 input logic Reset, Start;
9
10 // status signals
11 input logic exhaustedRAM, Found, gt;
12
13 // control signals
14 output logic Compute_M, Set_LSB, Set_MSB, init;
15
16 // define enum states
17 enum { idle, loop, done, wait1, wait2, wait3 = 6 } ps, ns;
18
19 // next state logic
20 always_comb begin
21   case(ps)
22     idle: ns = Start ? loop : idle;
23     loop: begin
24       if(exhaustedRAM)
25         ns = done;
26       else if(~exhaustedRAM & Found)
27         ns = done;
28       else if(~exhaustedRAM & ~Found)
29         ns = wait1;
30       end
31     wait1: ns = wait2;
32     wait2: ns = wait3;
33     wait3: ns = loop;
34     done: ns = done; // stay here until user presses Reset
35     default: ns = idle;
36   endcase
37 end
38
39 // controller logic with synchronous reset
40 always_ff @(posedge CLOCK_50) begin
41   if(Reset)
42     ps <= idle;
43   else
44     ps <= ns;
45   end
46 end
47
48 // output assignments
49 assign Compute_M = (ps == loop) & (gt | ~gt);
50 assign Set_MSB = (ps == loop) & ~gt;
51 assign Set_LSB = (ps == loop) & gt;
52 assign init = (ps == idle) & ~Start;
53
54 endmodule // binaryFSM
55

```

Figure 6: Snippet of module binaryFSM showing the control path for task 2

```

1 // Module to implement the data path portion of task 2; binary data search.
2 // CLOCK_50, Compute_M, Set_LSB, Set_MSB, init are single bit inputs.
3 // A is an 8 bit input
4 // Loc is a 5 bit output
5 // DONE is a single bit output
6 timescale 1 ps / 1 ps
7 module binaryDataPath (CLOCK_50, A, Compute_M, Set_LSB, Set_MSB, init, exhaustedRAM, gt, Found, Loc, DONE);
8
9 // external inputs
10 input logic CLOCK_50;
11 input logic [7:0] A;
12
13 // control signals (inputs)
14 input logic Compute_M, Set_LSB, Set_MSB, init;
15
16 // status signals (outputs)
17 output logic exhaustedRAM, gt, Found; // Found will also be an external output
18
19 // external outputs
20 output logic [4:0] Loc;
21 output logic DONE;
22
23 // internal variables
24 logic [4:0] LSB, MSB, M;
25 logic [7:0] q;
26 logic [7:0] target;
27
28 // datapath logic
29 always_ff @(posedge CLOCK_50) begin
30     if (init) begin
31         LSB <= 0;
32         M <= 5'd15;
33         MSB <= 5'd31;
34         target <= A;
35     end
36
37     if (Compute_M)
38         M <= (MSB + LSB) / 2;
39     if (Set_LSB)
40         LSB <= M + 1'b1;
41     if (Set_MSB)
42         MSB <= M - 1'b1;
43 end
44
45 // retrieve value to compare
46 RAM_32_8_1port RAM (.address(M), .clock(CLOCK_50), .data(0), .wren(0), .q(q));
47
48 assign exhaustedRAM = (MSB == LSB);
49 assign gt = (target > q);
50 assign Found = (target == q);
51 assign DONE = (MSB == LSB) | Found; // can be DONE without having found the target
52 assign Loc = M;
53
54 endmodule // binaryDataPath
55

```

Figure 7: Snippet of module *BinaryDataPath* showing the data path for task 2

 


Figure 8: Snippet of binary top-level model sim showing signal *F* as “1” at the correct .mif file index “1” where *A* = 5.

In ModelSim, we tested our binary search algorithm by assigning *A* a value and seeing if our algorithm could find a match to our target value. We initialized our RAM with multiples of 5, as seen in the snippet above to the right. We first tested a value that would not be in the RAM, which was *A* = 3, and we can see that *F* (Found) does not become asserted because it is never found in RAM, however *DONE* still asserts because it indicates that the algorithm has finished comparing all the elements in RAM to the target value. Next, we tested a value that was in RAM (*A* = 5), and we see that both *Found* and *DONE* are asserted as soon as our algorithm finds a match to our target.



## DE1\_SoC:

The top-level module of this lab is fairly straight forward. We simply assigned SW 0-7 to be our input to both algorithms and SW 9 to be the selector between the counter algorithm (task 1) and the binary search algorithm (task 2). We also had Key 0 as reset and Key 3 as Start to initiate our algorithms. In terms of algorithms instantiation, for counter algorithm, we made one instance of the counter control path and one instance of the counter data path and connected them together. For the binary search algorithm, we made one instance of the binary search control path and one instance of the data path and connected them together. Finally, we made 2 instances of the 7-segment display to show our counter value and the address that gets found by our binary search. We also included 2 LEDRs to demonstrate Done and Found status signals.

```

25 // assign the requested external inputs to the internal control signals.
26 assign A = sw[7:0];
27 assign Reset = ~KEY[0];
28 assign Start = ~KEY[3];
29 assign HEX5 = 7'h7F;
30 assign HEX4 = 7'h7F;
31 assign HEX3 = 7'h7F;
32 assign HEX2 = 7'h7F;
33
34 // initialize the counter algorithm FSM and datapath.
35 counter_ctrl cc(.clk(CLOCK_50), .reset(Reset), .s(Start), .A_zero, .got_1, .load_A, .r_shift_A, .incr_result, .clr_result, .done);
36 counter_datapath cdp (.clk(CLOCK_50), .A, .load_A, .r_shift_A, .incr_result, .clr_result, .A_zero, .got_1, .result);
37
38 // initialize the binary search algorithm FSM and datapath.
39 binaryFSM bc (.CLOCK_50, .Reset, .Start, .exhaustedRAM, .Found, .gt, .Compute_M, .Set_LSB, .Set_MSB, .init);
40 binaryDataPath bdp (.CLOCK_50, .A, .Compute_M, .Set_LSB, .Set_MSB, .init, .exhaustedRAM, .gt, .Found, .Loc, .DONE);
41
42 // switch between tasks
43 always_comb begin
44     case(sw[9])
45         0: // counter
46             begin
47                 out1 = result;
48                 out2 = 4'b0000;
49                 d = done;
50                 f = 0;
51             end
52         1: // binary search
53             begin
54                 out1 = Loc[3:0];
55                 out2 = {3'b0, Loc[4]};
56                 d = DONE;
57                 f = Found;
58             end
59         default:
60             begin
61                 out1 = result;
62                 out2 = 4'b0000;
63                 d = done;
64                 f = 0;
65             end
66     endcase
67 end
68
69 // initialize a seven segment display module that outputs either the counter value or address of target value.
70 seg7 seg1(.hex(out1), .leds(HEX0));
71 seg7 seg2(.hex(out2), .leds(HEX1));
72
73 assign LEDR[9] = d; // indicates done state for either counter or binary
74 assign LEDR[0] = f; // off for counter, used for binary to indicate Found
75
76 endmodule // DEL_Soc

```

Figure 9: DE1 SoC top level module

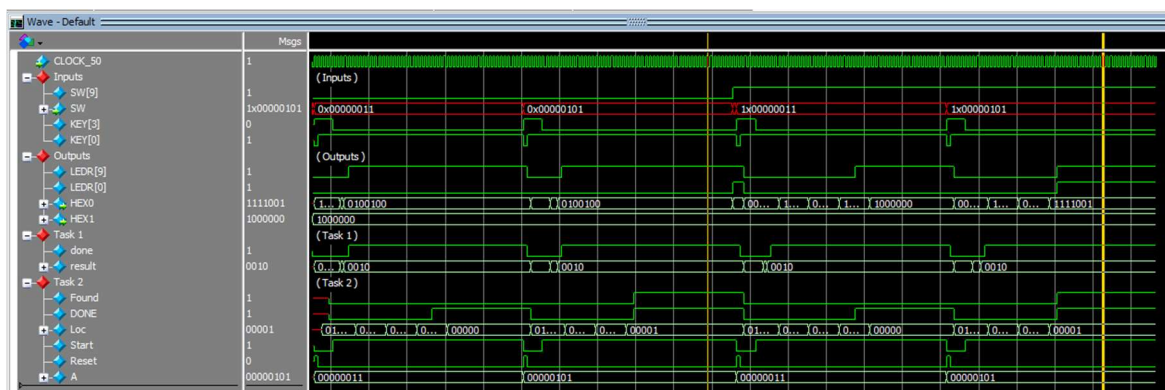


Figure 10: Snippet of DE1 SoC top level model sim showing the combined behaviour for task 1 and 2

For the top-level simulation, we combined the counter and the binary search testbench with the additional control of switching between the two algorithms at halfway point through the simulation. In the above ModelSim snippet, 2 yellow lines can be seen indicating the 2 points where the finished algorithm displays the final value. When SW[9] is set to 0, the counter algorithm is being selected and the result signal shows the value 2 since 2 input bits are set to 1. When SW[9] is set to 1, the binary search algorithm is being selected and the Loc signal shows the correct index when the value  $A = 5$  is located as previously shown in the mif file. The LEDRs and HEX displays also display the appropriate behavior for both algorithms as shown in the above snippet. The Start, Done, Reset signals are all correct and behave as expected.

## Flow Summary:

Flow Summary	
<<Filter>>	
Flow Status	Successful - Mon Nov 06 16:13:31 2023
Quartus Prime Version	17.0.0 Build 595 04/25/2017 SJ Lite Edition
Revision Name	DE1_SoC
Top-level Entity Name	DE1_SoC
Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	43 / 32,070 ( < 1 % )
Total registers	41
Total pins	67 / 457 ( 15 % )
Total virtual pins	0
Total block memory bits	256 / 4,065,280 ( < 1 % )
Total DSP Blocks	0 / 87 ( 0 % )
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 ( 0 % )
Total DLLs	0 / 4 ( 0 % )

Figure 11: Snippet of the Flow Summary for the top-level module DE1\_SoC

## Experience Report:

Implementing the 2<sup>nd</sup> task; binary search algorithm was relatively difficult. We initially encountered issues with identifying which signals are control vs status signals. We also encountered problems with getting the DE1\_SoC top level module to work on LabsLand. We also spent a lot of time determining if the ASMD components are combinational or sequential. We had to review the class lecture slides multiple times throughout working on the lab. For teamwork, we used GitHub for easy collaboration of shared files which made code developing and debugging more efficient. It was not very helpful to reference the provided block diagrams since they were incomplete and confusing. For the next lab we would like to get a head start and aim to work together live more frequently to reduce debugging time. Additionally, using GitHub's full functionality for version control may help make our code development process even smoother.

The estimated total time working on this lab was 24 hours broken as follows:

- Reading: 2 hours



- Planning: 2 hours
- Design: 5 hours
- Coding: 6 hours
- Testing: 5 hours
- Debugging: 4 hours.